

DARRELL ER (COPYRIGHTED) ©

“What one man calls God, another calls the laws of physics.”

-Nikola Tesla

TOPIC 18: D.C CIRCUITS

THE ABOUT

CHAPTER ANALYSIS



TIME

- Build up from Current Electricity
- 2 **major key** concepts
- Series Circuit, Parallel Circuit



EXAM

- Really need to practice to master the topic
- **Important** to get foundation right from Current Electricity



WEIGHTAGE

- Heavy-Medium overall weightage
- Constitute to around **5%** of marks for past 5 year papers


KEY CONCEPT

CIRCUIT DIAGRAM

SERIES CIRCUIT

PARALLEL CIRCUIT



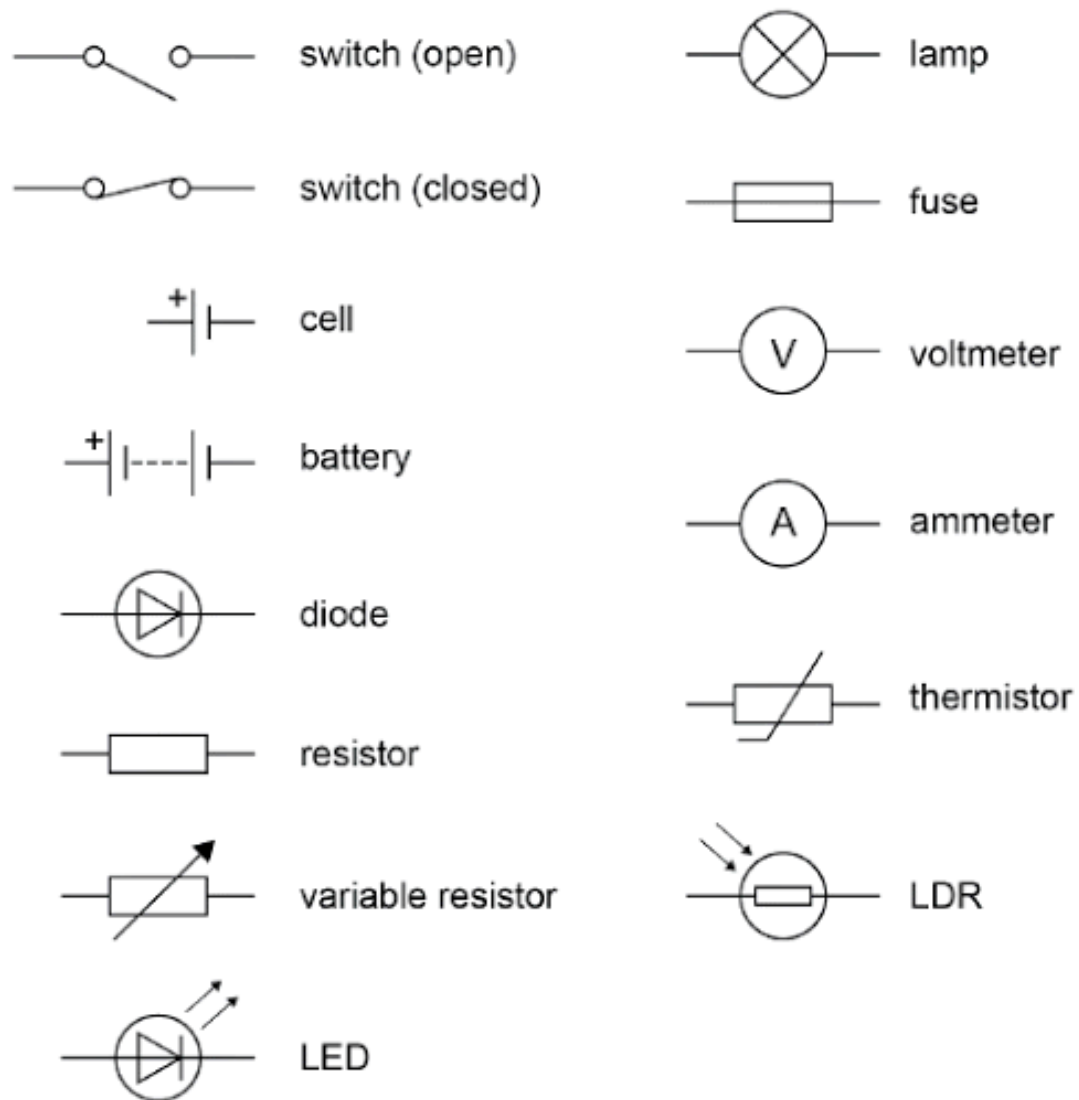

CIRCUIT DIAGRAMS

Familiarise yourself with the different components and their symbols!

Series


Parallel

Current


Current is the same throughout circuit.

Total current is sum of current in each separate branch.

$$I_1 = I_2 = I_3$$

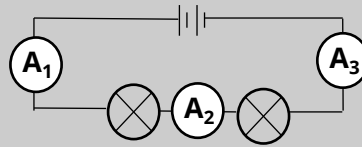

$$I_{\text{total}} = I_1 + I_2 + I_3$$

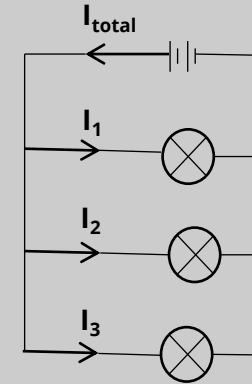


Potential Difference


Total P.D is sum of P.D across each component.



Potential difference is the same across each branch.

$$V_{\text{total}} = V_1 + V_2$$

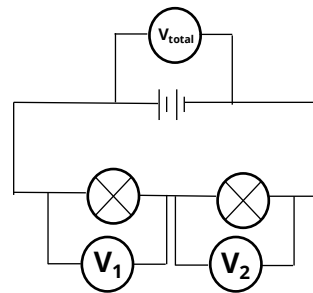


$$V_{\text{total}} = V_1 = V_2 = V_3$$

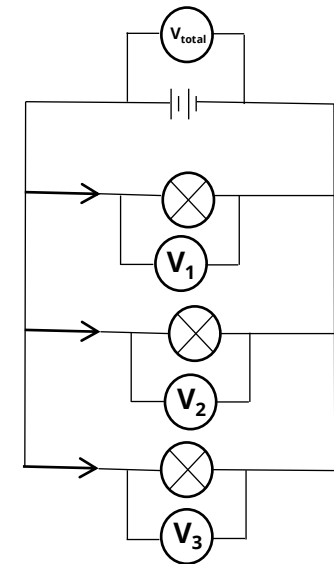
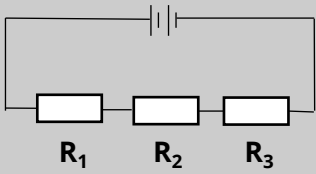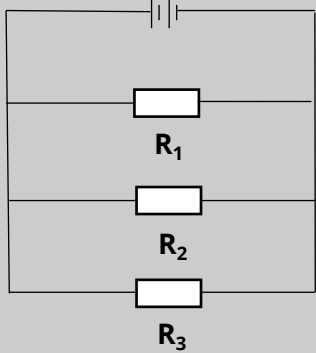
| | Series | Parallel |
|------------|--|---|
| Resistance | <p>Total effective resistance is sum of individual resistance.</p> $R_{\text{total}} = R_1 + R_2 + R_3$  | <p>Total effective resistance is sum of reciprocal of resistance in each branch.</p> $1 / R_{\text{total}} = 1/R_1 + 1/R_2 + 1/R_3$  |

VISUALISATION

A RIVER

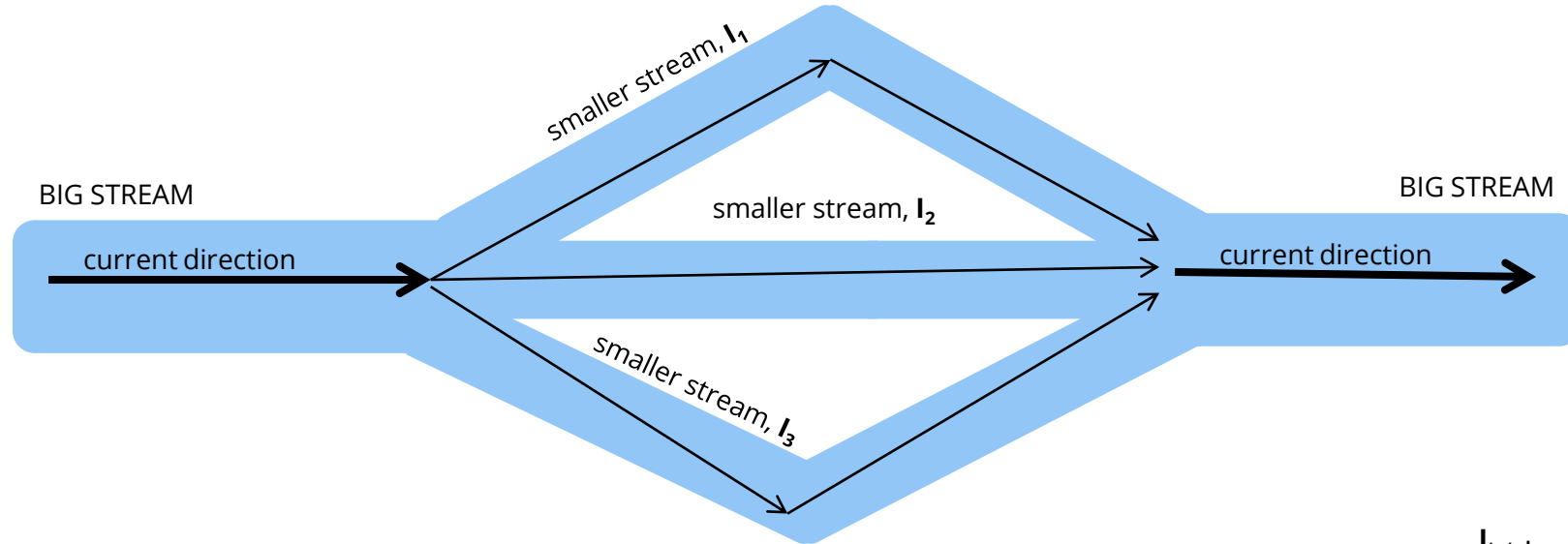

How electricity works in a circuit is similar to a river.


Current flows in a river and at times, it can split into smaller streams.

When it does, the volume of water is reduced in each smaller stream.


A parallel circuit works in the same way!

Current will split into smaller volume as it enters each individual branch of the circuit.

$$I_{\text{total}} = I_1 + I_2 + I_3$$

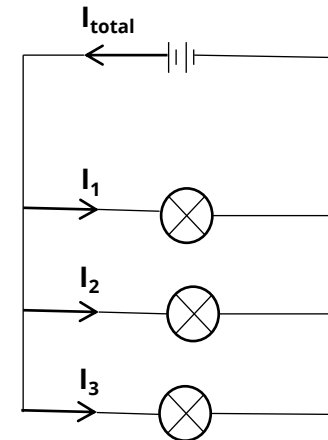


SERIES CIRCUIT

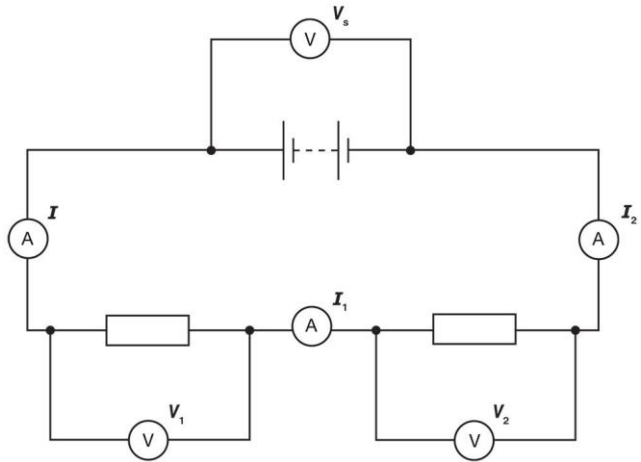

A **disadvantage** is that when one light bulb were to fuse, the entire circuit will no longer work.

SERIES CIRCUIT


Current is the same throughout circuit.

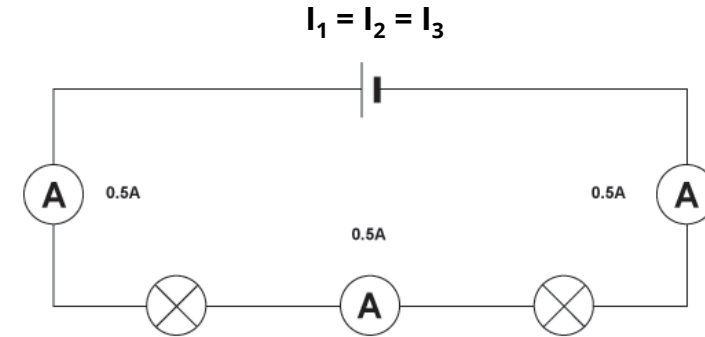

(There is only 1 big stream for the river)


Total potential difference is **sum of P.D** across each **component**, as the current has to pass through all the resistors.

$$V_{\text{total}} = V_1 + V_2$$

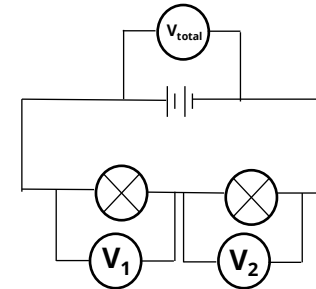


Total effective resistance is **sum of individual resistance**, as current has to pass through all the resistors.

$$R_{\text{total}} = R_1 + R_2 + R_3$$

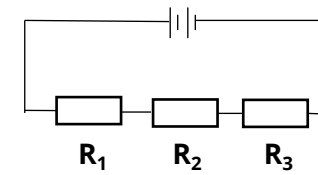

PARALLEL CIRCUIT

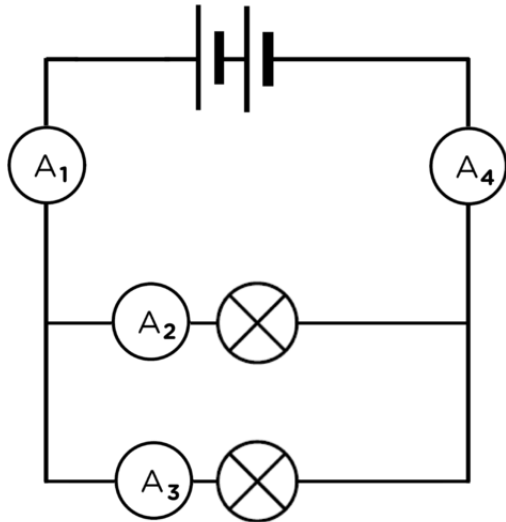


An **advantage** is that when one light bulb were to fuse the other parallel branches will still work.

PARALLEL CIRCUIT

Total current is sum of current in each separate branch.


$$I_{\text{total}} = I_1 + I_2 + I_3$$

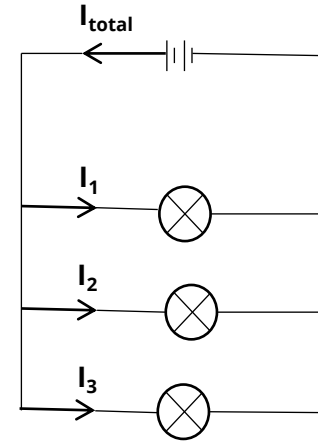

(River splits into smaller streams, current will get divided as well)

Potential difference is the same across each branch.

$$V = V_1 = V_2 = V_3$$

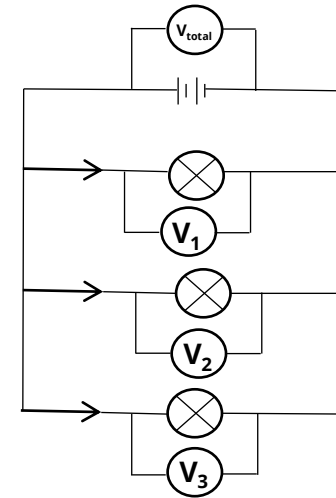


Total effective resistance is sum of reciprocal of resistance in each branch.

$$1 / R_{\text{total}} = 1/R_1 + 1/R_2 + 1/R_3$$

VISUALISATION

AN IMPORTANT CONCEPT

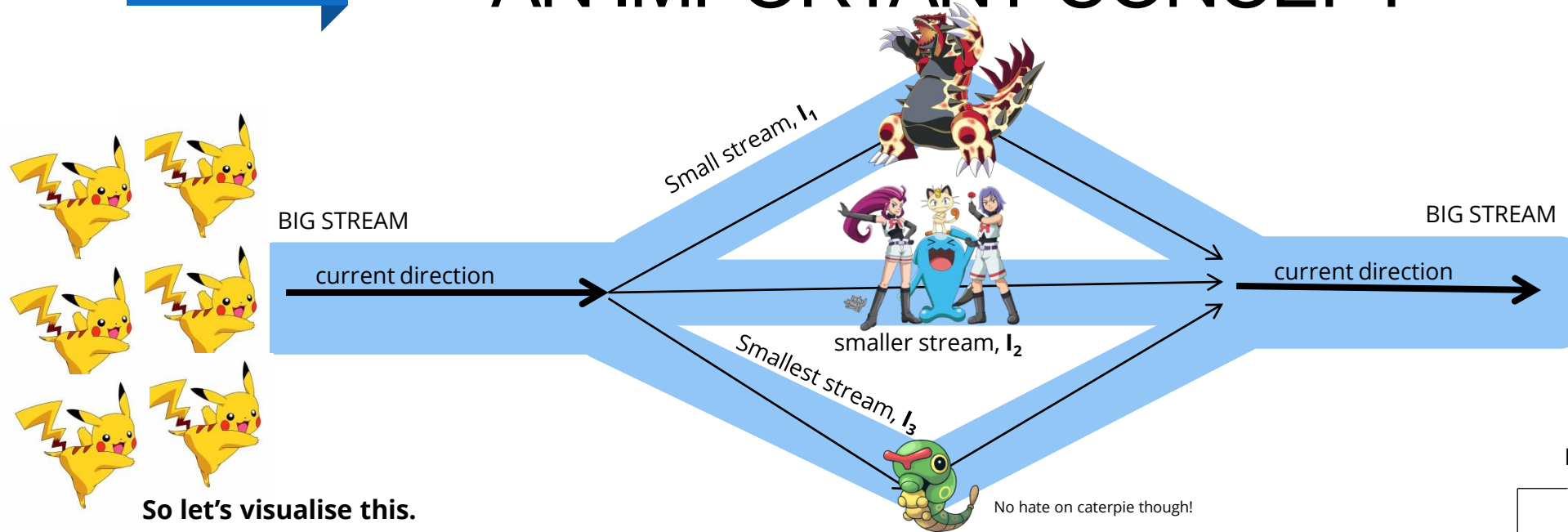

So let's visualise this.

This group of pikachu are the charges flowing in the river (current).

They have 3 *options*, which path do you reckon they will take?

Like most lazy humans, its will be the ***path of least resistance!***


Most pikachu will go down stream I_3 .

Some will go to stream I_2 .

Only a few will go to stream I_1 .

As current is the rate of flow of charges and charges tend to take the path of least resistance,

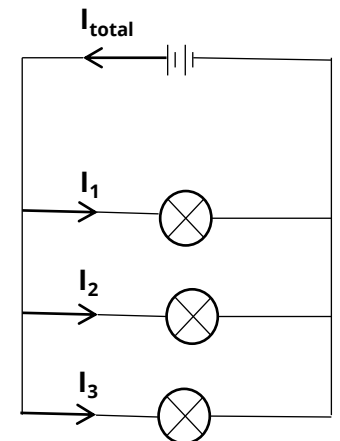
Current will split differently into each stream based on the amount of resistance in that branch.



$I_1 = I_2 = I_3$ **only when the resistance in each branch happens to be the same!**

PRACTICE QUESTION

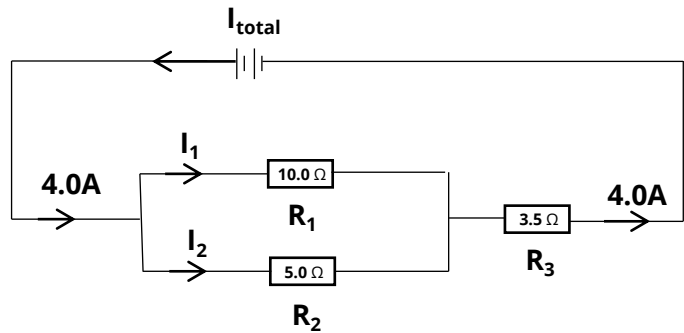How would the current split in this situation?



RECALL

Current will split into different branches in parallel circuit.

$$I_{\text{total}} = I_1 + I_2 + I_3$$

Due to path of resistance,

Current will split differently into each stream based on the amount of resistance in that branch.

HOW DO WE SOLVE THE QUESTION?

Recall that voltage across each parallel branch is constant, so since $V = RI$,

$$I_1 R_1 = I_2 R_2$$

$$I_1 \times 10.0 \Omega = I_2 \times 5.0 \Omega$$

$$2(I_1) = I_2$$

I_2 is twice the value of I_1 .

$$I_{\text{total}} = I_1 + I_2$$

$$4.0 \text{ A} = I_1 + 2(I_1)$$

$$I_1 = 4.0 \text{ A} / 3$$


$$I_1 = 1.3 \text{ A}$$

$$I_2 = 4.0 \text{ A} - 1.3 \text{ A} = 2.7 \text{ A}$$

PARALLEL IN SERIES


Using the same question, let's explore the resistance.

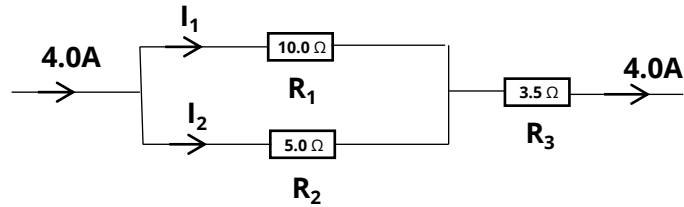This is a case of a **parallel in a series circuit**.




HOW DO WE SOLVE FOR THE EFFECTIVE RESISTANCE?

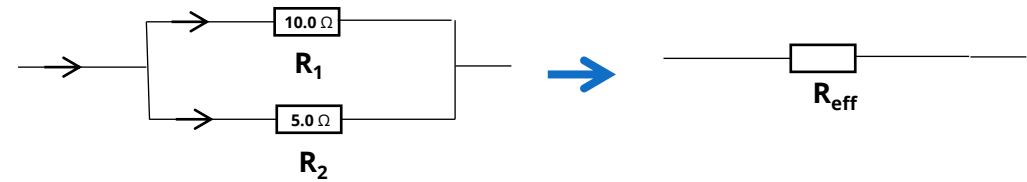(Combined R_1 & R_2 to simplify the circuit)



$$\begin{aligned} 1/R_{\text{eff}} &= 1/R_1 + 1/R_2 \\ 1/R_{\text{eff}} &= 1/10.0 + 1/5.0 \\ R_{\text{eff}} &= 3.33 \Omega \end{aligned}$$

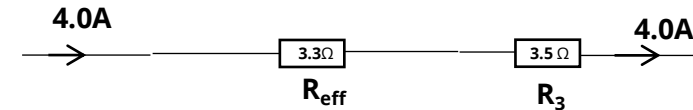(Since R_{eff} & R_3 are now technically in series)




$$R_{\text{total}} = 3.33 \Omega + 3.5 \Omega = 6.83 \Omega$$

HENCE, MAKE THE PARALLEL INTO A SINGLE RESISTOR BEFORE CALCULATING TOTAL RESISTANCE.


SERIES IN PARALLEL

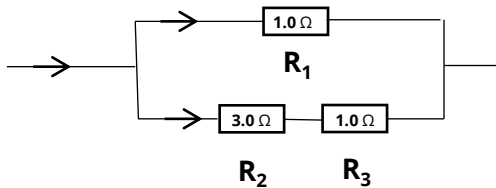There is also series in parallel **circuit**.



HOW DO WE SOLVE FOR THE EFFECTIVE RESISTANCE?

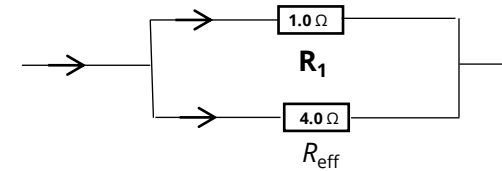(Combined $R_{3.0}$ & $R_{1.0}$ to simplify the circuit)



$$R_{\text{eff}} = 3.0 \, \Omega + 1.0 \, \Omega = 4.0 \, \Omega$$

(Since R_{eff} & R_3 are now technically in parallel)

$$\begin{aligned} 1/R_{\text{total}} &= 1/R_{1.0} + 1/R_{\text{eff}} \\ 1/R_{\text{total}} &= 1/1.0 + 1/4.0 \\ R_{\text{total}} &= 0.8 \, \Omega \end{aligned}$$

HENCE, MAKE THE SERIES INTO A SINGLE RESISTOR BEFORE CALCULATING TOTAL RESISTANCE.

For more notes & learning materials, visit:
www.overmugged.com

'O' levels crash course program

Professionally designed crash course to help you get a **condensed revision** before your 'O' Levels!

The **4 hour session** focuses on going through **key concepts** and **identifying commonly tested questions!**

Our **specialist tutors** will also impart valuable **exam pointers and tips** to help you maximise your preparation and ace your upcoming national exam!

The crash courses will begin in **June 2021** and last till **Oct 2021**.

Pre-register now on our [website](http://www.overmugged.com) and secure your slots!



IG handle:
[@overmugged](https://www.instagram.com/overmugged)



Join our telegram
channel:
[@overmugged](https://t.me/overmugged)



Need help?

Darrell Er
(Private tutor with **8**
years of experience)

8777 0921
(Whatsapp)

[@DarrellEr](https://t.me/DarrellEr)
(telegram username)



OVERMUGGED

FREE NOTES | CRASH COURSES | 'O' LEVELS | 'A' LEVELS

WWW.OVERMUGGED.COM